

Analog Electronics

angeloperotti7

February 2025

0.1 Introduction

- mail: philippe.velha@unitn.it
- exam
 - written: mandatory, 0-30
 - lab reports: mandatory, pass-no pass
 - spice project: optional but is extra credit
 - assignments: design and spice simulations (optional but gives extra credit)
- main arguments
 - course introduction
 - rectification block
 - regulation block
 - transistor block
 - opamp block
 - protection and integration
- books:
 - art of electronics
 - ...

Chapter 1

fundamentals

1.1 theory introduction

1.1.1 Voltage

- intended as potential difference between two points
- the voltage difference between two points is the work required in Joules to move one Coulomb of charge from A to B
- $1V = 1 \frac{J}{C}$
- voltage is expressed in Volts

1.1.2 Current

- is the rate of flow of electric charges past a point around a closed circuit
 - *point* is not precise – > we will define a point as an average through said checkpoint
 - rate implies an average over time: $I = \frac{N \cdot q}{\Delta t} = \frac{Q}{t}$
- Current is measured in Amperes [A]
- corresponds to the flow of 1 Coulomb of charge per second
- definition of current density= J , $I = \int \int J \cdot dA$

1.1.3 sources of Voltage and Current

- Independent voltage sources
- real voltage sources
- independent current sources
- real current sources

1.1.4 Power

- Power is energy per unit time
- $P = V \cdot I$
- $\frac{\text{energy}}{\text{charge}} \cdot \frac{\text{charge}}{\text{time}}$
- expressed in watts [W]= $1 \frac{J}{s}$
- power is sometimes dissipated in heat or in mechanical work of some type

1.2 Fundeamental Laws

1.2.1 Mawell Equations

- $\nabla \cdot E = \frac{\rho}{\epsilon}$: Gauss'law
- Gauss' law for magnetism
- Faraday's law of induction
- Ampere's Law

1.2.2 kirchoff

KCL

- Ω : a volume containing a node
- S ; surface boundary of Ω
- S_K : intersection between and wire k
- n_K : normal of surface S_K

$$\int \int_{\Omega} \nabla \cdot J dV = \int \int_S J \cdot ndS = \sum_{k=1}^N \int \int J \cdot ndS + \int \int_{S/\cup_{k=1}^N}$$

KVL

1.3 Elementary linear components

1.3.1 Capacitor

1.3.2 Inductance

1.3.3 Resistorns

1.4 types of signals

1.5 Thevenin theorem

any two-terminal network whose internal circuitry consists solely of resistors, batteries, and current sources, interconnected in any manner whatsoever, is equivalent (and indistinguishable) from the two-terminal network consisting of a single battery V_{TH} in series with a single resistor R_{TH}

1.6 Amplifiers

1.6.1 models of the amplifiers

- Voltage Amplifier
 - Gain parameter
 - * Open circuit voltage gain
 - * $A_{v_0} \equiv \frac{v_0}{v_i} \big|_{i_0=0} \quad (V/V)$
 - Ideal Characteristics
 - * $R_i = \infty$
 - * $R_0 = 0$
- current amplifier
 - Gain parameter
 - * Short-circuit Current gain

- * $A_{is} \equiv \frac{i_0}{i_i} \big|_{v_0=0} \quad (A/A)$
- Ideal Characteristics
 - * $R_i = 0$
 - * $R_0 = \infty$
- Transconductance amplifier
 - Gain parameter
 - * short-circuit transconductance
 - * $G_m \equiv \frac{i_0}{v_i} \big|_{v_0=0} \quad (A/V)$
 - Ideal Characteristics
 - * $R_i = \infty$
 - * $R_0 = \infty$
- transresistance amplifier
 - Gain parameter
 - * Open circuit transresistance
 - * $R_m \equiv \frac{v_0}{i_i} \big|_{i_0=0} \quad (V/A)$
 - Ideal Characteristics
 - * $R_i = 0$
 - * $R_0 = 0$

1.6.2 unilateral amplifier

- signal flows in only one direction
- it is a model used sometimes to indicate that input and output are totally isolated
- this for the sake of modelling simplifies greatly but might not be always true

1.6.3 Frequency response

- a sinewave applied to a linear circuit is transformed in another sinewave with a different amplitude and some phase shift.

1.6.4 Single time constant networks (STC)

- minimum STC network is a resistor and reactive load (capacitor or inductor)
- usually classified in 2 categories LP(low pass) and HP(high pass)
- an STC circuit formed of an inductance L and a resistance R has a time constant $\tau = L/R$
- the time constant τ of an STC circuit composed of a capacitance C and a resistance R is given by $\tau = RC$
- time constant evaluation
 - The first step in the analysis of an STC circuit is to evaluate its time constant τ (unit: seconds)
 - in many instances, it will be important to be able to evaluate rapidly the time constant τ of a given STC circuit.
 - A simple method for accomplishing this goal consists first of reducing the excitation to zero; that is, if the excitation is by a voltage source, short it, and if by a current source open it!

classification of STCs

- Low-Pass
- High-Pass